




## Introduction To Sensors – Lesson 5: Infrared Encoder

### SCHEMATICS

The following schematic material is meant to go with the online lesson found here:  
[http://www.pyroelectro.com/edu/sensors/infrared\\_encoder/](http://www.pyroelectro.com/edu/sensors/infrared_encoder/)
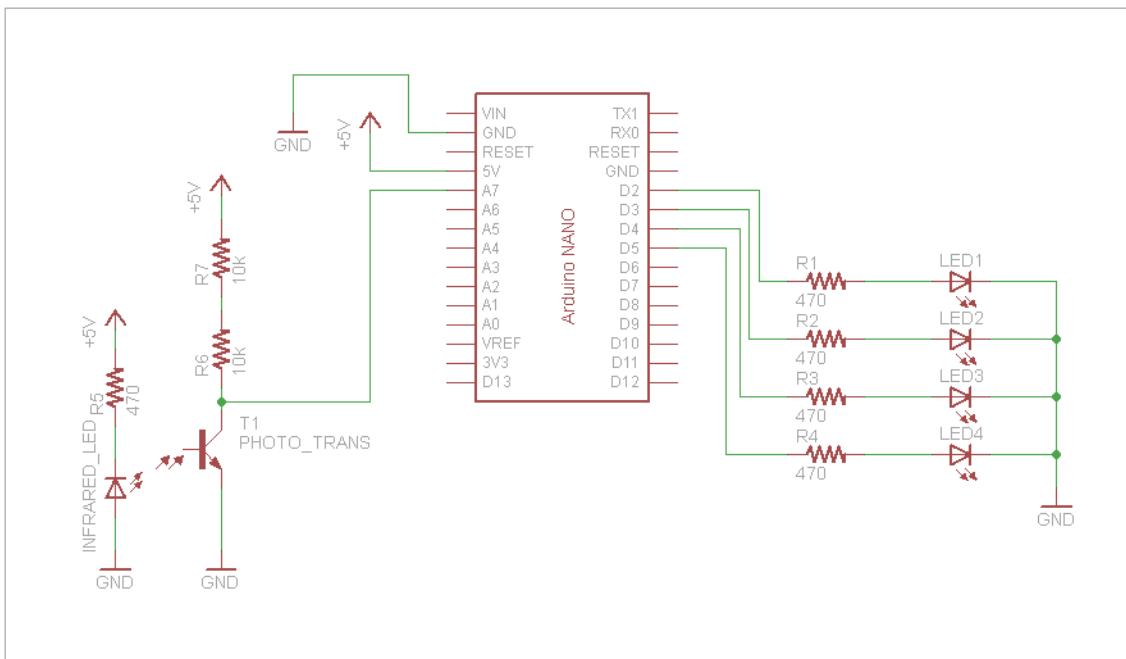
## LESSON 5 SCHEMATIC

The lesson 5 schematic uses an infrared emitter and phototransistor to make the encoder sensor and then 4 red leds to output when transitions are detected:



In this lesson the infrared encoder was used to track the different transitions between detecting white color and black color. This allowed us to track the movement of an encoder wheel!

### ADDITIONAL INFORMATION

To ask questions about anything found in this schematic please head on over to the forums located at:  
<http://www.pyroelectro.com/forums/viewforum.php?f=27>