



# PyroElectro.com - PyroEDU

*Introduction To Digital Electronics – Lesson 3: Logic Gates*

## HOMEWORK

The following homework questions are meant to go with the online lesson found here:  
[http://www.pyroelectro.com/edu/digital/logic\\_gates/](http://www.pyroelectro.com/edu/digital/logic_gates/)

### HOMEWORK QUESTION 1

What are the 3 basic logic gates of digital electronics? What are their logic symbols?

### HOMEWORK QUESTION 2

How are the 3 basic logic gates (answer from question 1) different from one another?

### HOMEWORK QUESTION 3

Using X and Y as input variables and Z as an output variable, write the three Boolean algebra equations that represents the 3 basic logic gates.

### HOMEWORK QUESTION 4

What information does a truth table tell us about a logic gate?

### ADDITIONAL INFORMATION

To get feedback on your homework or to ask additional questions related to this lesson, please post your homework answers or your questions in the online forums at:  
<http://www.pyroelectro.com/forums/viewforum.php?f=21>