



PyroElectro.com - PyroEDU


Introduction To Sensors – Lesson 6: Sound Sensor

SCHEMATICS

The following schematic material is meant to go with the online lesson found here:
<http://www.pyroelectro.com/edu/sensors/sound/>

LESSON 6 SCHEMATIC

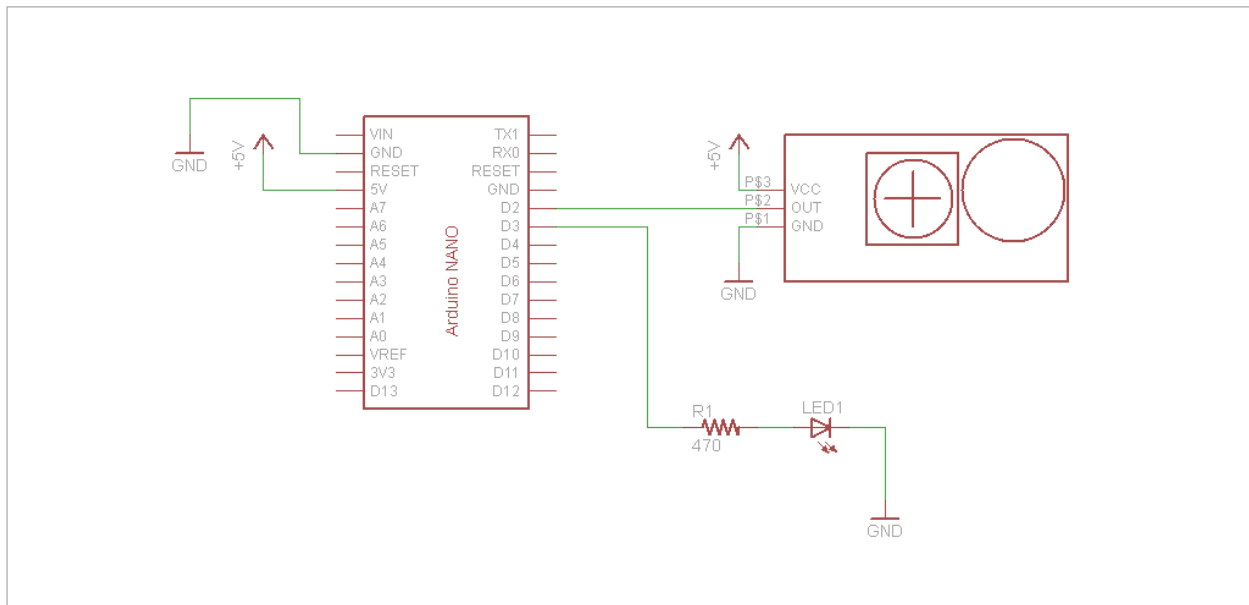The lesson 6 schematic consists of three main elements, the sound sensor, the arduino nano and the LED indicator:



In this lesson we programmed the arduino nano so that everytime the sound sensor sent an interrupt signal we blinked the LED a few times to create a visual indication!

ADDITIONAL INFORMATION

To ask questions about anything found in this schematic please head on over to the forums located at:

<http://www.pyroelectro.com/forums/viewforum.php?f=27>